

Voltage vs. Current for R_1 and R_2 for parallel

