

# Lab 2 Simple DC Circuits

Philip Kim

February 23, 2021

Table 1: Voltage vs. Current for  $R_1$

	1	2	3	4	5	6
Voltage (V)	1.12	2.02	2.99	3.95	5.07	6.09
Current (I)	0.056	0.103	0.148	0.198	0.250	0.308

$$R_1 = \boxed{19.97 \pm 0.25\Omega} \quad (1)$$

Table 2: Voltage vs. Current for  $R_2$

	1	2	3	4	5	6
Voltage (V)	1.06	1.89	3.12	3.97	4.88	5.90
Current (I)	0.043	0.079	0.132	0.165	0.200	0.249

$$R_2 = \boxed{24.06 \pm 0.4\Omega} \quad (2)$$

Table 3: Voltage vs. Current for  $R_1$  and  $R_2$  in series

	1	2	3	4	5	6
Voltage (V)	0.91	2.09	3.08	3.98	5.01	5.97
Current (I)	0.021	0.048	0.071	0.091	0.114	0.133

$$\begin{aligned} R_S &= R_1 + R_2 \\ &= \boxed{44.03 \pm 0.65\Omega} \end{aligned} \quad (3)$$

Table 4: Voltage vs. Current for  $R_1$  and  $R_2$  in parallel

	1	2	3	4	5	6
Voltage (V)	0.93	2.12	3.10	4.10	5.11	5.99
Current (I)	0.0841	0.1930	0.2880	0.3800	0.4740	0.5540

$$\begin{aligned} R_P &= \frac{R_1 * R_2}{R_1 + R_2} \\ &= \boxed{10.91 \pm 0.15\Omega} \end{aligned} \quad (4)$$

1. Consider the diagram of the experiment Fig. 2.2 and the real life situation. Are your calculated values for the unknown resistances slightly larger or slightly smaller than the actual unknown resistance? Explain.
  - The calculated values are slightly larger because resistance is directly proportional to the temperature and increased temperature will lead to an increase in resistance.
2. We have tried to keep the currents low in this experiment, what are the various things that could occur if the current is allowed to be larger?
  - By using low current, we can avoid a larger increase in resistance of wire.