

# Lab 6: The Impedance of Capacitors

Philip Kim

March 10, 2021

## Part 1

Table 1: Impedance of a Capacitor										
C	R	$V_{RC}$	$V_R$	V/DIV for $V_R$	$f_{gen}$	$f_{osc}$	$I_R$	$V_C$	$X_{C,exp}$	$X_{X,the}$
$0.22\mu F$	$1k\Omega$									
$0.33\mu F$	$1k\Omega$									
$0.10\mu F$	$1k\Omega$									
$0.47\mu F$	$1k\Omega$									
$0.68\mu F$	$1k\Omega$									
$1.00\mu F$	$1k\Omega$									

Picture 1

Graph 1

Graph 2

Discussion 1

1. What slope do you find for graph 2 and how does it compare to your expectation?
  -
2. What does a deviation from the linear fit indicate? How would you correct for the ones with the largest error?
  -