

Lab 7: The DIY Capacitor

Philip Kim

March 25, 2021

Part 1


Table 1: Geometry of the Capacitor

| | |
|-------------------|------|
| Width 1 w_1 | 6" |
| Width 2 w_2 | 6" |
| Area of overlap A | 276" |

Table 2: Impedance the DIY Capacitor

| n | R | V_{RC} | V_R | V/DIV for V_R | f_{gen} | f_{osc} | I_R | V_C | $X_{C,exp}$ |
|-----|------|----------|-------|-----------------|-----------|-----------|--------|--------|-------------|
| 1 | 470Ω | 4.54V | 3.97V | 2V | 2023Hz | 2052Hz | 0.0084 | 2.2024 | 260.74 |
| 2 | 470Ω | 4.54V | 3.89V | 2V | 2023Hz | 2052Hz | 0.0083 | 2.3408 | 282.83 |
| 3 | 470Ω | 4.54V | 3.65V | 2V | 2023Hz | 2052Hz | 0.0078 | 2.6998 | 346.65 |
| 4 | 470Ω | 4.54V | 3.48V | 2V | 2023Hz | 2052Hz | 0.0074 | 2.9157 | 393.78 |
| 1 | 470Ω | 4.54V | 4.05V | 2V | 2023Hz | 2052Hz | 0.0086 | 2.0516 | 238.09 |
| 2 | 470Ω | 4.54V | 3.89V | 2V | 2023Hz | 2052Hz | 0.0083 | 2.3408 | 282.83 |
| 3 | 470Ω | 4.54V | 3.73V | 2V | 2023Hz | 2052Hz | 0.0079 | 2.5882 | 326.13 |
| 4 | 470Ω | 4.54V | 3.40V | 2V | 2023Hz | 2052Hz | 0.0072 | 3.0086 | 415.89 |
| 1 | 470Ω | 4.54V | 3.89V | 2V | 2023Hz | 2052Hz | 0.0083 | 2.3408 | 282.83 |
| 2 | 470Ω | 4.54V | 3.65V | 2V | 2023Hz | 2052Hz | 0.0078 | 2.6998 | 346.65 |
| 3 | 470Ω | 4.54V | 3.56V | 2V | 2023Hz | 2052Hz | 0.0076 | 2.8174 | 371.97 |
| 4 | 470Ω | 4.54V | 3.40V | 2V | 2023Hz | 2052Hz | 0.0072 | 3.0086 | 415.89 |


V_{RC} Setup

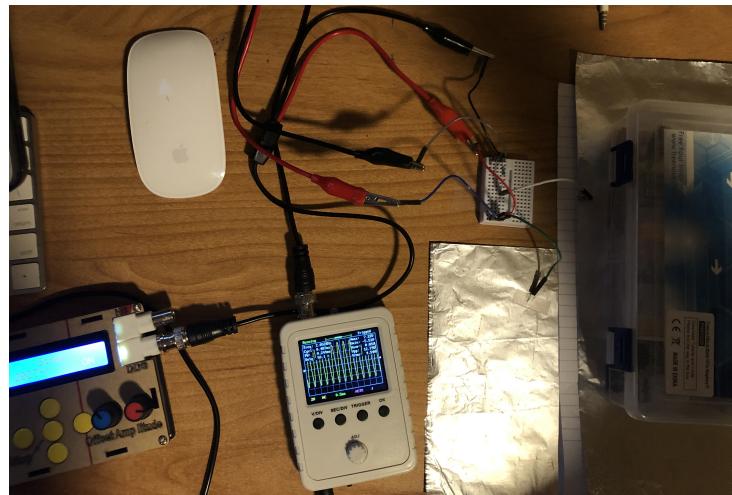


V_R Setup



Graph 1:

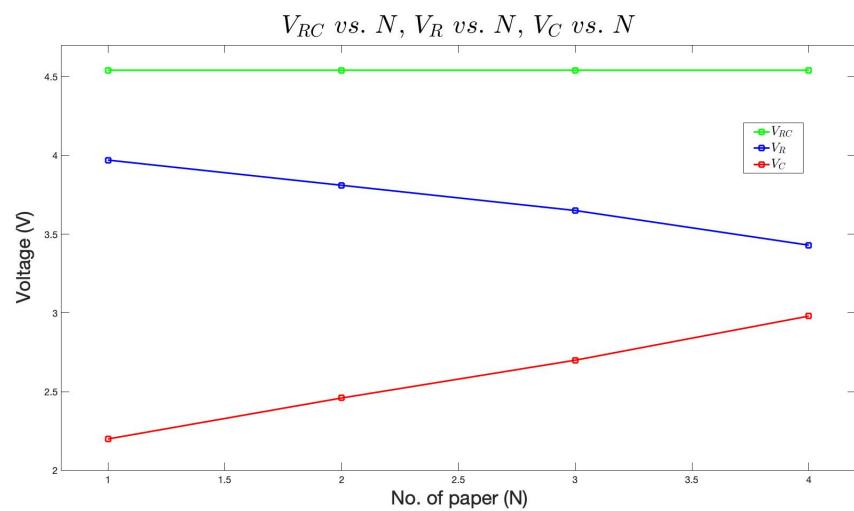

Graph 2:

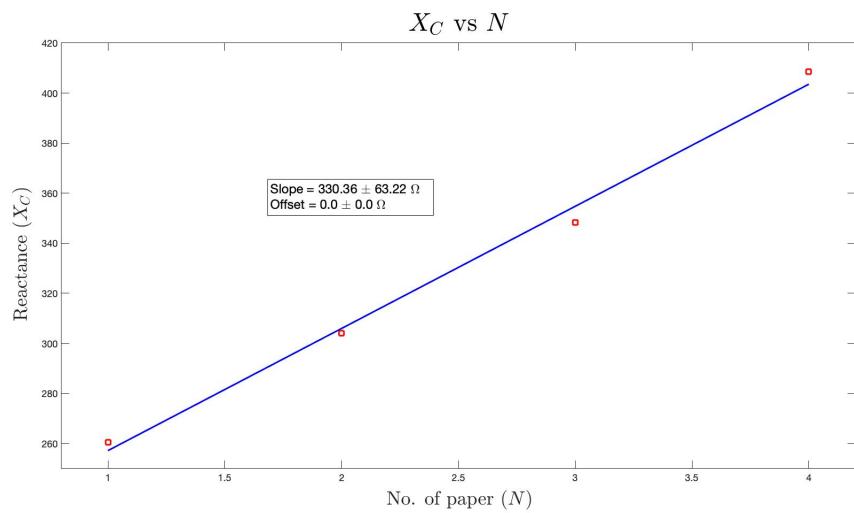

1. What slope do you find for graph 2 and how does it compare to your expectation?
 - Slope = $330.36 \pm 63.22 \Omega$
 - Expectation = $0.0 \pm 0.0 \Omega$
2. What do you think could cause the offset in the fit?
 - Mostly from the aluminum foil not being constant and always changing its form.